
 
 
 






Lab 7: OTA DESIGN

Part 1: g_m / I_D design charts:

For NMOS, design charts:

 

For PMOS, design charts:

    

We used NMOS input stage, as we can see that the range of the V_{INCM} is close to V_{DD} and away from ground.

Detailed design procedure and hand analysis:

Input pair:

$$A_o = \frac{g_{m0,1} r_o}{2} = 34 \text{ dB} \therefore g_{m0,1} r_o = 100.2$$

Sweeping the DC gain over g_m over I_D then we got the value of L , $L = 460 \text{ nm}$

$$GBW = \frac{g_{m0,1}}{2\pi C_L} = 10 \text{ MHz} \therefore g_{m0,1} = 100\pi \mu\text{S}$$

Assume $g_m/I_D = 5\pi = 15.7 \text{ V}^{-1}$

Then $I_D / W = 1 \mu\text{A}/\mu\text{m}$ Then $W = 16.6 \mu\text{m}$

But after design we found that $W = 20 \mu\text{m}$ is the most suitable value for the input pair

We got the value of:

$$V_{GS} = 827 \text{ mV} \quad V_{DSAT} = 105 \text{ mV}$$

Cascode PMOS devices:

Assume $g_m/I_D = 15 \text{ V}^{-1}$, $g_m = 300 \mu\text{S}$, and we have the value of r_o from the previous design, then $g_{m2,3} r_o = 95.68$

Now we got the value of L , $L = 380 \text{ nm}$.

Using the spec: $V_{IN,MAX} \geq 1.5$:







$$V_{IN,MAX} = V_{DD} - V_{SG} + V_{GS} - V_{DSAT} \geq 1.5$$

$$1.8 - 1.5 + 0.827 - 0.103 \geq V_{SG}$$

Then $1.023 \geq V_{SG}$

we got the right value of g_m / I_D , $g_m / I_D = 8$.

      Then $I_D / W = 2.679 \mu\text{A}/\mu\text{m}$ Then $W = 8 \mu\text{m}$



Current mirror sizing:

$$CMRR = \frac{g_{m0,1} r_o}{2} 2g_{m2,3} r_{o5}, \therefore r_{o5} = 312562 \text{ ohm}$$

Assume $g_m/I_D = 15 \text{ V}^{-1}$, $g_{m5} = 600 \mu\text{S}$

$$\therefore g_{m5} r_{o5} = 187 \quad L = 640 \text{ nm}$$

Using the spec: $V_{IN,MAX} \leq 1$:

$$V_{IN,MIN} = V_{GS} + V_{DSAT,5} \leq 1$$




Then $0.173 \geq V_{DSAT}$

we got the right value of g_m / I_D , $g_m / I_D = 13$.

Then $I_D / W = 0.442 \mu\text{A}/\mu\text{m}$ Then $W = 90 \mu\text{m}$


Now we can deduce the size of the reference device M4:
   
$$L = 640 \text{ nm} \quad W = 90 / 4 = 23 \mu\text{m}$$



	M0	M1	M2	M3	M4	M5
W	20 μm	20 μm	8 μm	8 μm	23 μm	90 μm
L	460 nm	460 nm	380 nm	380 nm	640 nm	640 nm
g_m	$100\pi \mu\text{S}$	$100\pi \mu\text{S}$	$300 \mu\text{S}$	$300 \mu\text{S}$	$520 \mu\text{S}$	$520 \mu\text{S}$
I_D	20 μA	20 μA	20 μA	20 μA	10 μA	40 μA
g_m / I_D	$5\pi \text{ V}^{-1}$	$5\pi \text{ V}^{-1}$	8 V^{-1}	8 V^{-1}	13 V^{-1}	13 V^{-1}
V_{DSAT}	103 mV	103 mV	219 mV	219 mV	123 mV	123 mV
V_{OV}	29 mV	29 mV	296 mV	296 mV	97 mV	97 mV
V^*	127 mV	127 mV	250mV	250mV	153 mV	153 mV

Part 3: OTA OPEN LOOP SIMULATION:

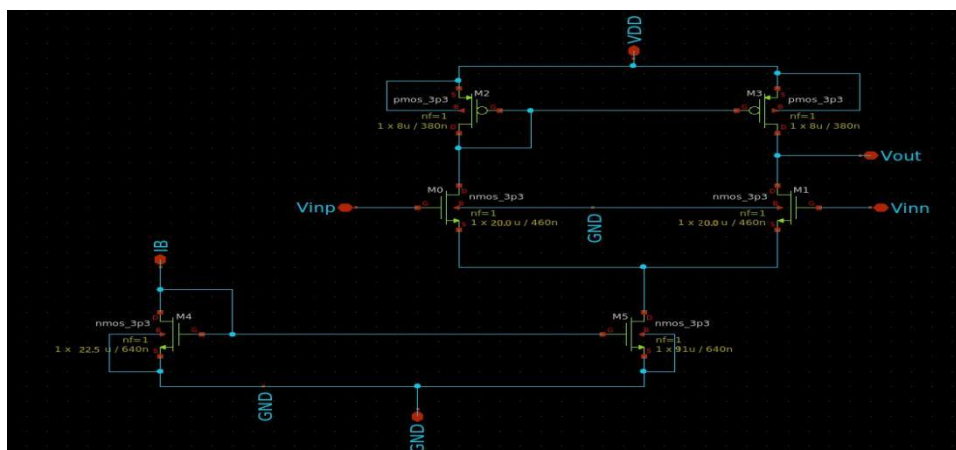

```

f2 = 1.567980e+05
peak = 6.399306e+01
f2 = 1.567980e+05
gbw = 1.003398e+07
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm4.m0      m.x1.xm5.m0      m.x1.xm3.m0
model      nmos_3p3.13      nmos_3p3.13      pmos_3p3.8
gm          0.000183113    0.000725042      0.000156271
gmbs       6.74608e-05     0.000267011      6.34088e-05
gds        8.37325e-07     4.13585e-06      1.71904e-06
vds        0.694392       0.402934         0.985093
vdsat      0.0810139      0.080989         0.220791
vgs        0.694393       0.694393         0.985097
vth        0.702963       0.70302          0.774523
id         1e-05          3.94006e-05      1.97003e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm2.m0      m.x1.xm1.m0      m.x1.xm0.m0
model      pmos_3p3.8      nmos_3p3.12      nmos_3p3.12
gm          0.000156271    0.000321908      0.000321908
gmbs       6.34088e-05     8.93451e-05      8.93451e-05
gds        1.71904e-06     3.28371e-06      3.28371e-06
vds        0.985093       0.411962         0.411962
vdsat      0.220791       0.0974711        0.0974711
vgs        0.985097       0.847064         0.847064
vth        0.774523       0.830341         0.830341
id         1.97003e-05     1.97003e-05      1.97003e-05

binary raw file "OTA_TB.raw"
ngspice 1 ->


```

from these results, we can see that I_D and g_m of the input pairs are exactly equal, and the reason for that is that if we assumed the current is high in a branch, then it is should be low in the other branch, but this assumption always wrong, so they are equal.

- the DC voltage at $V_{out} = V_{DS,0} + V_{DS,5} = 0.813 \text{ V}$

Diff small signal:

Diff gain VS freq:

 

```

f2 = 1.607189e+05
peak = 6.225101e+01
f2 = 1.607189e+05
gbw = 1.000491e+07

```

Hand analysis calculation:

$$A_{vd} = g_{m0,1} (r_{o3} // r_{o1}) = 321 \times 10^{-6} \times (304878 // 584795) = 64.32 = 36 \text{ dB}$$


$$BW \approx \frac{1}{2\pi C_L (r_{o3} // r_{o1})} \approx \frac{1}{2\pi \times 5 \times 10^{-12} \times (304878 // 584795)} \approx 158.83 \text{ kHz}$$

$$GBW = A_{vd} \times BW = \frac{g_{m0,1}}{2\pi C_L} = \frac{1}{2\pi \times 5 \times 10^{-12}} = 10.21 \text{ MHz}$$

	Analytical solution	Simulation
DC gain	64.32 36 dB	62.25 35.88 dB
Band width	158.83 kHz	160.7 kHz
GBW	10.21 MHz	10.04 MHz

CM small signal:

CM gain VS freq:

 

```
f2 = 1.609154e+05
peak = 9.192579e-03
f2 = 1.609154e+05
gbw = 1.479228e+03
```

Hand analysis calculation:

$$A_{vcm} \approx \frac{-1}{2g_{m2,3}r_{o5}} \approx \frac{-1}{2 \times 156 \times 10^{-6} \times 241837} = -12.8 \times 10^{-3} = -37.8 \text{ dB}$$


$$BW = \frac{1}{2\pi C_L (r_{o3} // r_{o1})} \approx \frac{1}{2\pi \times 5 \times 10^{-12} \times (304878 // 584795)} \approx 158.83 \text{ kHz}$$

$$GBW = |A_{vcm}| \times BW = 12.8 \times 10^{-3} \times 158.83 = 2025 \text{ Hz}$$

	Analytical soltution	Simulation
DC gain	0.0128 -37.8 dB	0.00919 -40.73 dB
Band width	158.83 kHz	160.9 kHz
GBW	2.02 kHz	1.47 kHz

CMRR simulation:

CMRR vs frequency:

 

$$\text{CMRR} = \frac{A_{vd}}{A_{vcm}} = g_{m0,1} (r_{o3} // r_{o1}) \cdot 2g_{m2,3} r_{o5} = 5016 = 74 \text{ dB}$$

	Analytical soltution	Simulation
CMRR	5016 74 dB	6760 76.6 dB


Diff large signal analysis:

V_{OD} vs V_{ID} :




At $V_{ID} = 0$, $V_{OD} = 0.813$ V

Derivative of V_{OD} VS V_{ID} :

 


CM large signal:

GBW vs V_{INCM} :

 

```
No. of Data Rows : 111
diffgain      = 3.815597e-01 at= 1.000000e+00
f3db          = 6.080836e+06
Warning from checkvalid: vector vicm is not available or has zero length.
Error: RHS "vact + vicm" invalid
binary raw file "OTA.raw"
vicmmax = 1.620000e+00
vicmmin = 8.100000e-01
ngspice 1 -> █
```

Part 4: closed_loop OTA simulation:

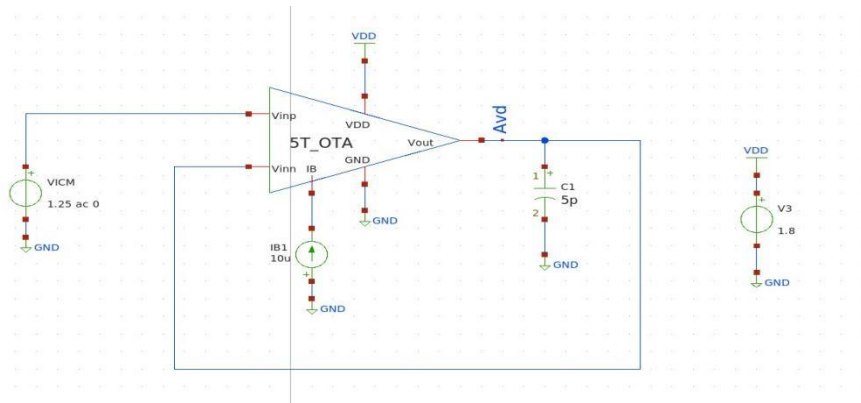

```

device      m_x1.xm4.m0      m_x1.xm5.m0      m_x1.xm3.m0
model       rmos_3p3.13      rmos_3p3.13      pmos_3p3.8
gm          0.000169102      0.000664931      0.000155517
gmbs        6.22864e-05      0.000244836      6.32366e-05
gds         7.61485e-07      3.66347e-06      2.57079e-06
vds         0.716397        0.444546        0.507385
vdsat       0.0913748      0.0913479      0.214834
vgs         0.716398        0.716398        0.979592
vth         0.702959        0.703012        0.776451
id          1e-05           3.91443e-05      1.90823e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m_x1.xm2.m0      m_x1.xm1.m0      m_x1.xm0.m0
model       pmos_3p3.8      rmos_3p3.12      rmos_3p3.12
gm          0.000162764      0.000316257      0.000327548
gmbs        6.60272e-05      8.50252e-05      8.81051e-05
gds         1.7678e-06      2.59167e-06      3.70461e-06
vds         0.979588        0.848059        0.375855
vdsat       0.216179        0.0945382      0.0976603
vgs         0.979592        0.84806        0.855452
vth         0.774755        0.837224      0.838437
id          2.0062e-05      1.90823e-05      2.0062e-05

gm_mismatch = 1.129160e-05
id_mismatch = 9.797114e-07


```

From these results, it is clear that I_D and g_m for input pairs are not equal, and the reason for that is node of output no longer follow the drain node of the other input pair, then the current will be different because of CLM that make the current has some dependence on V_{DS} , then g_m will be different, too. That case is opposite to OTA open loop case, as output node was following the drain node of the i/p pair.


$$\text{Mismatch in } g_m = \frac{327 - 321}{321} * 100 = 1.869\% \quad \text{Mismatch in } I_D = \frac{1.97 - 2.0062}{1.97} * 100 = 1.83\%$$

Where $g_m = 321 \mu S$ is the nominal value, and $I_D = 1.97 \mu A$ is the nominal value.


Loop gain (PM and GM):

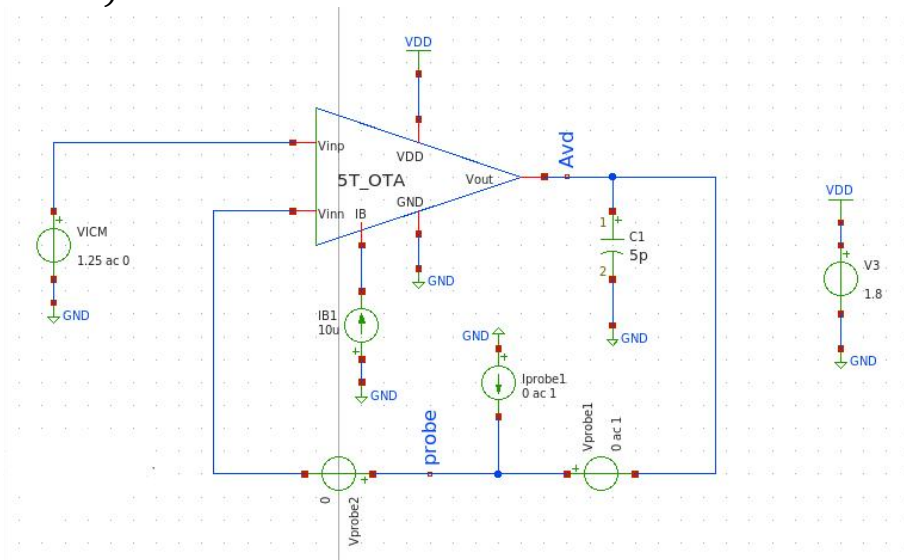


Loop gain vs frequency:

 

Phase vs frequency:

 

Phase and mag (overlaid) vs frequency:

 

Results and OP Point:

```
peak = 6.277052e+01 at= 2.238721e+00
Error: measure f1 when(WHEN) : out of interval
meas ac f1 when vmag(mb)=4.438546e+01 rise=1 failed!

bw = 1.562775e+05
pm_deg = -8.963814e+01
dominant_pole_f = 9.812251e+05
loop_gain = 3.535511e+01
gbw = 9.809620e+05
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
device m.x1.xm4.m0 m.x1.xm5.m0 m.x1.xm3.m0
model nmos_3p3.13 nmos_3p3.13 pmos_3p3.8
gm 0.000169102 0.000652842 0.000153354
gmbs 6.22864e-05 0.000244055 5.33958e-05
gds 7.61485e-07 3.85137e-06 2.39666e-06
vds 0.716337 0.405886 0.55647
vdsat 0.0913748 0.091344 0.214312
vgs 0.716338 0.715398 0.978758
vth 0.702959 0.703019 0.776274
id 1e-05 3.89932e-05 1.90741e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device m.x1.xm2.m0 m.x1.xm1.m0 m.x1.xm0.m0
model pmos_3p3.8 nmos_3p3.12 nmos_3p3.12
gm 0.00016219 0.000315131 0.000326149
gmbs 6.57913e-05 8.648e-05 8.92431e-05
gds 1.75842e-06 2.59557e-06 3.46715e-06
vds 0.978754 0.837633 0.415343
vdsat 0.215514 0.0943304 0.0970518
vgs 0.978758 0.837635 0.844111
vth 0.774758 0.826951 0.828073
id 1.9325e-05 1.90741e-05 1.93255e-05
```

	Closed loop	Open loop
DC gain	62.7 35.95 dB	64.6 36.1 dB
GBW	9.81 MHz	10.04 MHz

```

No. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m,x1,xm4,m0      m,x1,xm5,m0      m,x1,xm3,m0
model       nmos_3p3,13     nmos_3p3,13     pmos_3p3,8
cgb         -1,25553e-14    -5,0755e-14     -1,8308e-15
cdb         -2,3104e-15    -9,37501e-15    -1,17457e-15
cgs         -1,37792e-14    -5,57728e-14    -6,84286e-15

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m,x1,xm2,m0      m,x1,xm1,m0      m,x1,xm0,m0
model       pmos_3p3,8     nmos_3p3,12     nmos_3p3,12
cgb         -1,84328e-15    -5,56407e-15    -5,47286e-15
cdb         -1,16234e-15    -1,21952e-15    -1,26571e-15
cgs         -6,83315e-15    -1,01801e-14    -1,05454e-14

```

Hand analysis calculations:

As we connected the gate of M1 with the output node, then parasitic capacitance will increase, which means that BW will decrease, then GBW will decrease.

$$A_{v-loop\ gain} = \beta A_{vd} = 321 \times 10^{-6} \times (418410 // 386100) = 63.45 = 36\text{ dB}$$

The equivalent output capacitance, $C_{out} = C_L + 2C_{gs,1} + C_{db,1} + C_{db,3} + C_{gb,1}$

We can see that there are additional parasitic caps.

$$BW \approx \frac{1}{2\pi C_{out}(r_{o3} // r_{o1})} \approx \frac{1}{2\pi \times 5.0315 \times 10^{-12} \times (304878 // 584795)} \approx 157.5\text{ kHz}$$

$$GBW = A_{vd} \times BW = \frac{g_{m0,1}}{2\pi C_{out}} = \frac{1}{2\pi \times 5.0315 \times 10^{-12}} = 9.995\text{ MHz}$$

	Hand analysis	simulation
DC gain	63.45 36 dB	62.7 35.95 dB
GBW	9.995 MHz	9.84 MHz